

ECE112 Lab Report - Linux and Spice Simulation lab

Jacob Reger

February 12, 2020

Lab 6a - ECE112

Here is what I did

This lab was about running the spice simulator and printing some results with latex. My results from this lab are shown in figure 1.

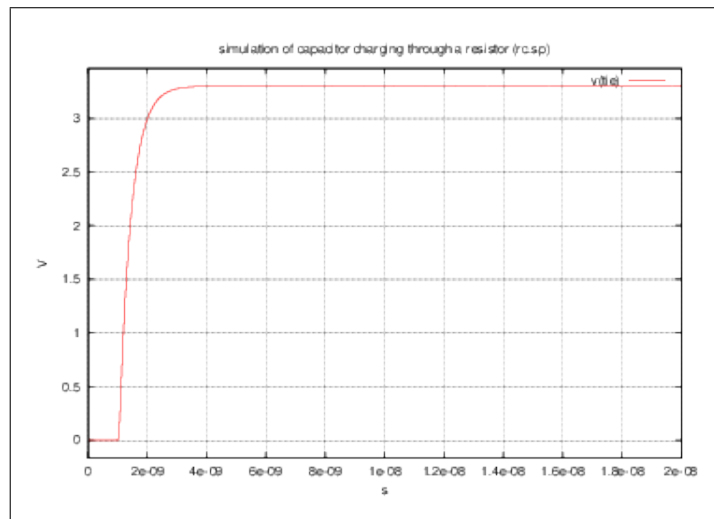


Figure 1: RC Simulation

Spice netlist

Here is the spice input file I used:

```
Simulation of capacitor charging through a resistor (rc.sp)

vsrvc vin 0 PULSE(0 3.3 1ns 100p 100p 100e-9 250e-9) ;voltage source
r1 vin tie 400 ;series resistor
*c1 tie 0 10pf ;capacitor to ground
c1 tie 0 1pf ;capacitor to ground

.control
set hcopydevtype=postscript
set hcopypscolor=0
set color0=rgb:f/f/f
set color1=rgb:0/0/0
tran 10ps 20ns
plot V(tie) xl 0.1ns 20ns
gnuplot sim_output V(tie) xl 10ps 20ns
.endc
.end
```

Signed: _____